



CPE 151/EEE 234
Digital IC Design


Project No. 2

Andrew Robertson
andrewrobertson@csus.edu
3/17/19


Table of Contents

2-Input NAND Schematic	3
2-Input NAND Symbol	4
2-Input NAND Testbench	5
Testbench Waveforms	6
2-Input NAND Layout	8
2-Input NAND DRC and LVS	9
2-Input NAND Extracted Parasitic Layout	11
Post Layout Response	12
Conclusion Table	13


2-Input NAND Schematic

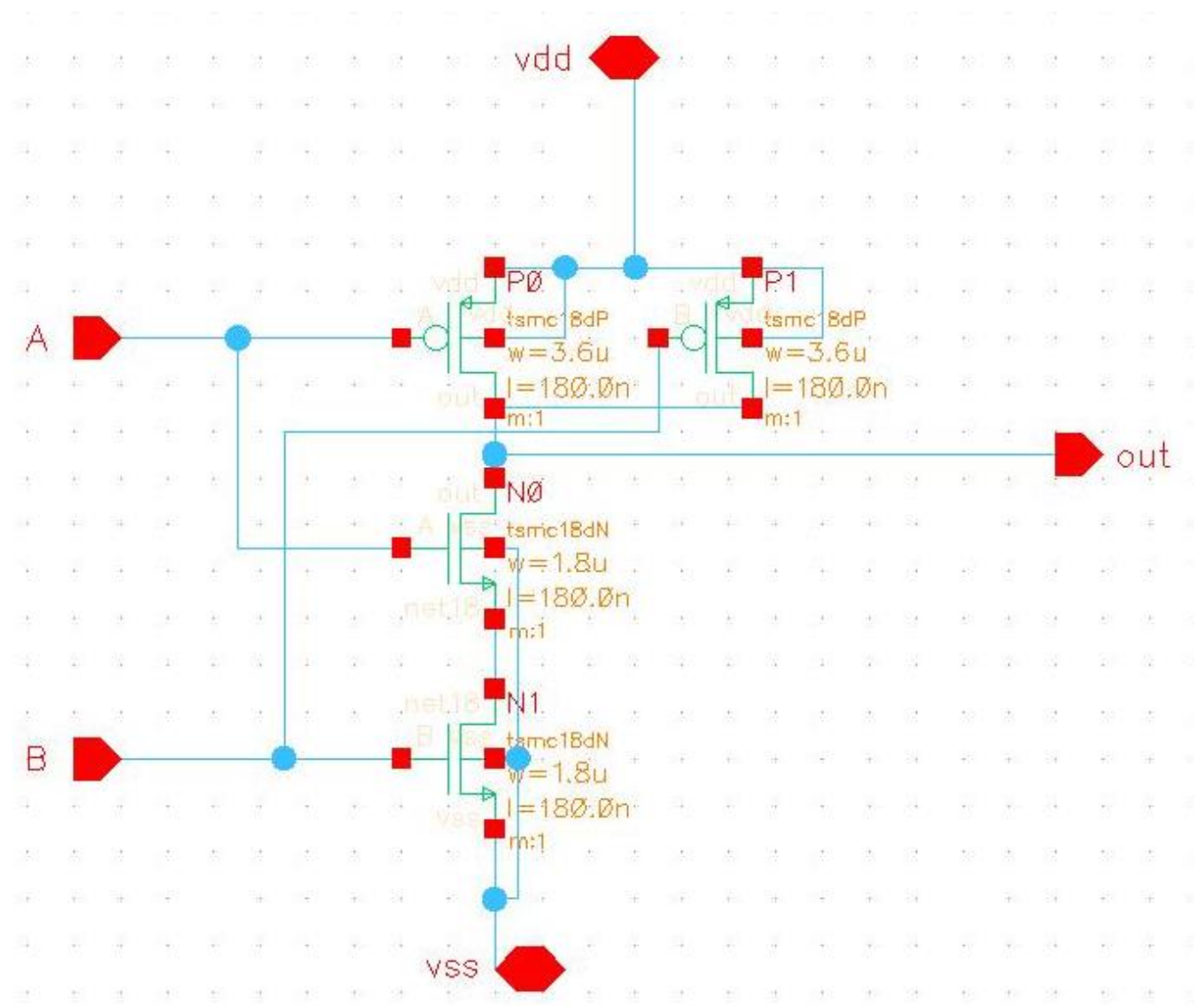

2-Input NAND Symbol

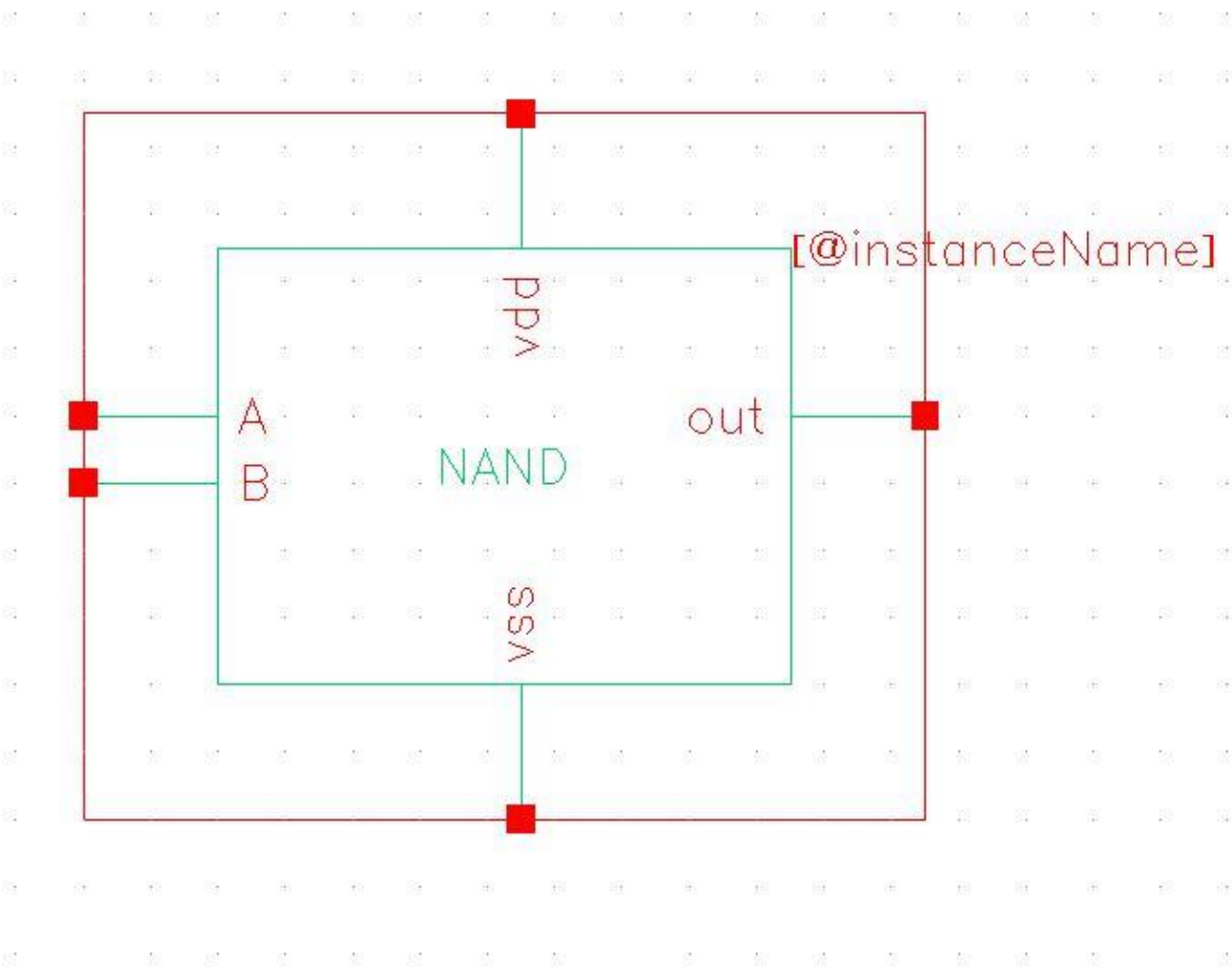

2-Input NAND Testbench

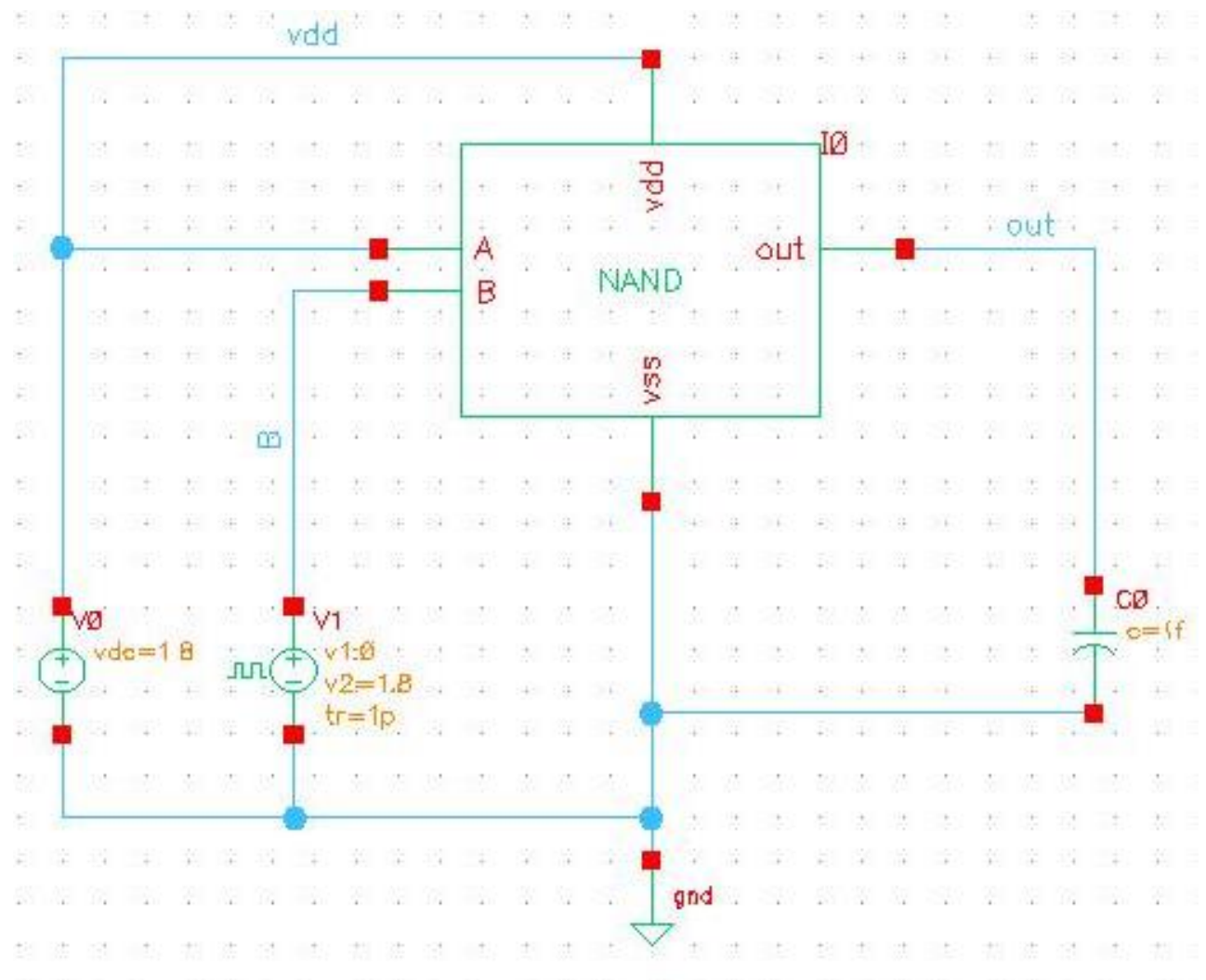


Testbench Waveforms

DrewProj2:sim_nand2_trans:1 : DrewProj2 sim_nand2_trans schematic

16:37:12 Fri Mar 15 2019

Transient Response

Fri Mar 15 16:18:03 2019

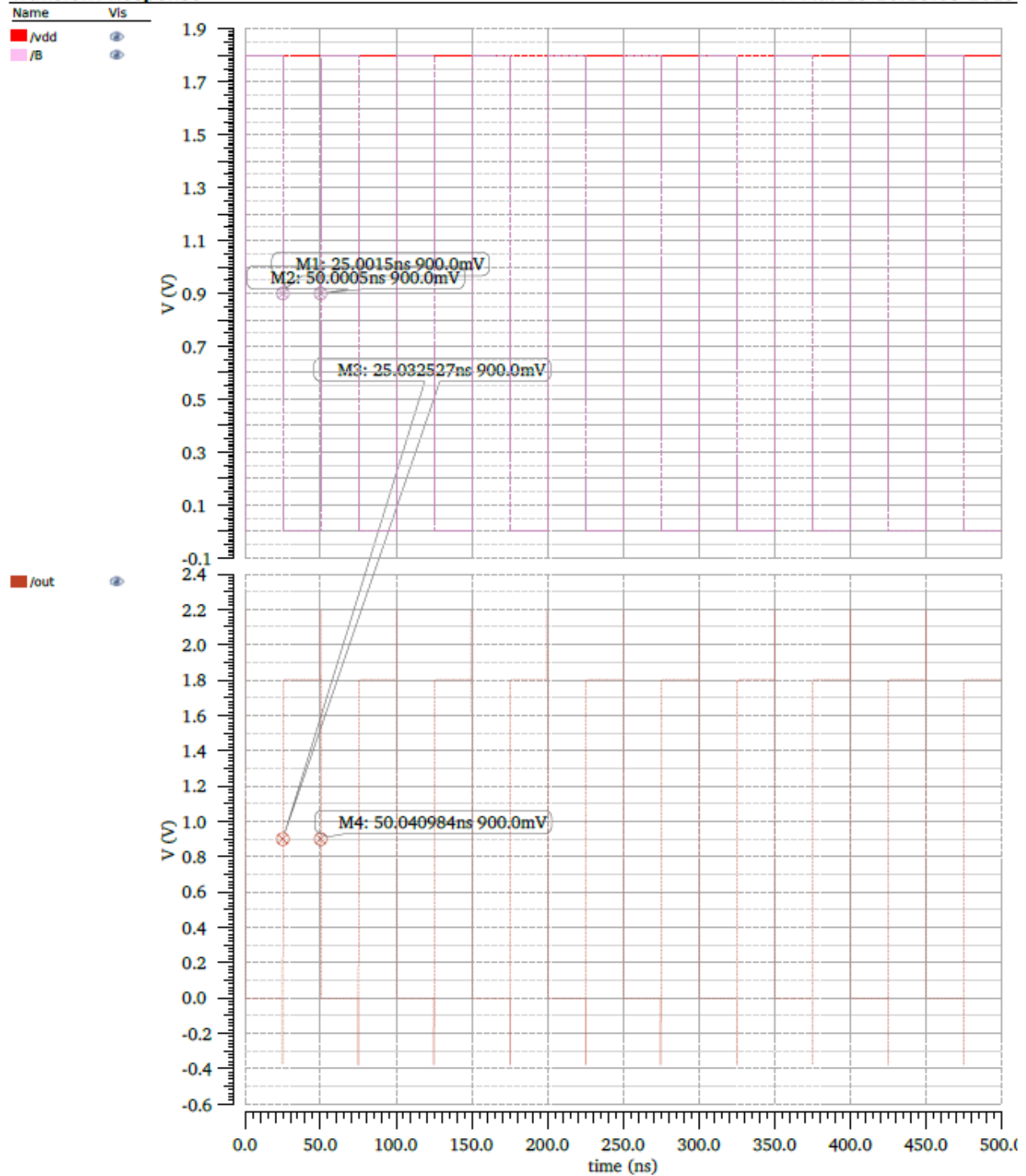


(A second one with the A input tied to ground instead of vdd)

Transient Response


Fri Mar 15 16:42:50 2019

Name	Vis
------	-----


█ /vdd	<input checked="" type="checkbox"/>
█ /B	<input checked="" type="checkbox"/>

 

█ /out	<input checked="" type="checkbox"/>
---	-------------------------------------

 

2-Input NAND Layout

 

2-Input NAND DRC and LVS

Running layout DRC analysis

Flat mode

Full checking.

DRC started.....Sun Mar 17 19:00:34 2019

completedSun Mar 17 19:00:34 2019

CPU TIME = 00:00:00 TOTAL TIME = 00:00:00

***** Summary of rule violations for cell "nand2_Layout layout" *****

Total errors found: 0

@(#)SCDS: LVS version 6.1.7-64b 09/27/2016 19:41 (sjfhw305) \$

Command line:

```
/software/cadence/installs/IC617/tools.lnx86/dfII/bin/64bit/LVS
-dir /gaia/class/student/robertsa/cadenceV/LVS -l -s -t
/gaia/class/student/robertsa/cadenceV/LVS/layout
/gaia/class/student/robertsa/cadenceV/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...
```

Net-list summary for
/gaia/class/student/robertsa/cadenceV/LVS/layout/netlist

count	
6	nets
5	terminals
2	pmos
2	nmos

Net-list summary for
/gaia/class/student/robertsa/cadenceV/LVS/schematic/netlist

count	
6	nets
5	terminals
2	pmos
2	nmos

Terminal correspondence points

N4	N1	A
N3	N5	B
N5	N4	out
N1	N2	vdd
N2	N0	vss

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	4	4
total	4	4
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	6	6
total	6	6
	terminals	
un-matched	0	0
matched but different type	0	0
total	5	5

Probe files from
/gaia/class/student/robertsa/cadenceV/LVS/schematic

devbad.out:

netbad.out:

mergenet.out:

termbad.out:

prunenet.out:

prunedev.out:

audit.out:

Probe files from
/gaia/class/student/robertsa/cadenceV/LVS/layout

devbad.out:

netbad.out:

mergenet.out:


termbad.out:

prunenet.out:

prunedev.out:

audit.out:

2-Input NAND Extracted Parasitic Layout

 

Post Layout Response


DrewProj2:sim_nand2_trans:1 : DrewProj2 sim_nand2_trans schematic

18:51:57 Sun Mar 17 2019

DC Response

Sun Mar 17 18:48:56 2019

Name	Vis
/out	<input checked="" type="checkbox"/>
/B	<input checked="" type="checkbox"/>

 

Conclusion Table

Description	Rise Time	Fall Time	Delay
2 input NAND	.031027ns	.040484ns	.0357555